

ELEKTROBOJ

Radionica: Glazbena olovka – od olovke do jednostavnog glazbala

KRATKE UPUTE

Davor Cihlar






Popis komponenti:

Molimo Vas da pregledate radno mjesto i stavite kvačicu kraj onih komponenata koje imate pred sobom. Ukoliko Vam nedostaje nešto od navedenoga, odmah recite.

Naziv:	Količina:	Potvrda:
Baterija 9V	1	
Konektor za 9V bateriju	1	
Integrirani krug TS555	1	
Podnožje za TS555	1	
Tranzistor BC546	1	
Tranzistor BC556	1	
Otpornik 8.2k Ω	1	
Otpornik 330k Ω	1	
Otpornik 100 Ω	1	
Elektrolitski kondenzator 100 μ F	1	
Keramički kondenzator 680pF	1	
Zvučnik	1	
Mala pločica za lemljenje	1	
Žice za spajanje		
Lemilica	1	
Tinol	1	

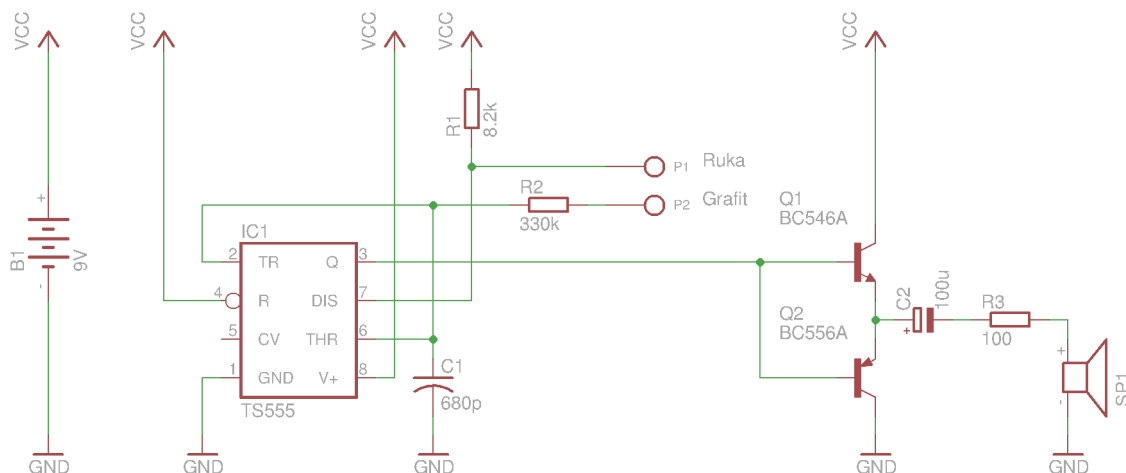

Slika 1. Shema

Proučite detaljno shemu! Ukoliko vam nešto nije jasno pozovite nekoga od nas i zatražite pomoć i dodatna pojašnjenja.

OBJAŠNJENE RADA:

Oscilator:

Srce sklopa je oscilator koji mijenja svoju frekvenciju u ovisnosti o otporniku spojenom na priključke P1 i P2 (nazovimo ga R_{EXT}). R_{EXT} ovisi o seriji otpora grafitu u olovci (nekoliko oma – zanemarivo), čovjeka (oko 200kΩ) i crteža (do 1MΩ na nekoliko centimetara). Crtež je jedina varijabilna vrijednost i o njemu će u konačnosti ovisiti frekvencija.

Oscilator je temeljen na vremenskom integriranom krugu TS555 (IC1) koji periodički puni i prazni kondenzator C1. C1 se puni preko serije otpornika R1, R_{EXT} i R2, a prazni preko serije otpornika R_{EXT} i R2. C1 se sporije puni zbog većeg otpora i kako bi trajanje punjenja bilo što bliže trajanju pražnjenja (*duty cycle* $\approx 50\%$) otpornik R1 mora biti što manji. Proizvoljno je odabran nekoliko reda veličine manji otpor od 8.2kΩ.

Formula za frekvenciju oscilatora je sljedeća:

$$f = \frac{1}{\ln(2) \cdot (R1 + 2(R2 + R_{EXT})) \cdot C1}$$

Uvrštavanjem vrijednosti otpornika u formulu za frekvencije 20Hz i 20kHz možemo zaključiti da bi nam za C1 pasao kondenzator od oko 680pF. R2 ograničava maksimalnu frekvenciju (pri $R_{EXT} = 0\Omega$) sa svojih 330kΩ na oko 20kHz.

Pojačalo:

Za maksimalnu snagu na zvučniku od 8Ω, 0.2W je potrebna struja od oko 160mA:

$$P = I^2 \cdot R \rightarrow I = \sqrt{\frac{P}{R}}$$

No TS555 na izlazu može dati svega desetak miliampera. Stoga je potrebno ubaciti pojačalo između zvučnika i vremenskog sklopa.

Pojačalo s dva tranzistora prikazano na shemi (Q1 i Q2) je jedno od najjednostavnijih. Sastoji se od pozitivnog i negativnog slijedila napona i stoga mu je naponsko pojačanje $\times 1$.

Korišteni su nešto slabiji tranzistori kako bi sklop bio jeftiniji i kako bi baterija duže trajala – nije

potrebna maksimalna glasnoća. U seriju sa zvučnikom je otpornik (R3) od 100Ω kako bi ograničio struju kroz zvučnik i smanjio opterećenje na tranzistorima koji ne mogu dati više od 100mA.

$$I = \frac{U}{R} = \frac{U_{BAT} - U_{BE}}{R3 + R_{SP1}} = \frac{9V - 0.7V}{100\Omega + 8\Omega} = 78mA$$


Osim otpornika u seriji sa zvučnikom se nalazi i elektrolitski kondenzator (C2). Njegova uloga je zaštita zvučnika od istosmjerne komponente iz pojačala. Kapacitet mora biti što veći kako bi impedancija pri 20Hz bila što manja.

SAVJETI:

- Prije samog lemljenja komponenata na pločicu, pregledajte shemu i napravite okvirni plan, tj. raspored komponenti na pločici. Time ćete si uštedjeti puno vremena i smanjiti mogućnost pogreške.
- Nikako nemojte stavljati žice preko integriranog kruga jer ga onda više neće biti moguće lako zamijeniti.

U dodatku se nalaze ključne stranice iz tehničkih dokumentacija svih poluvodičkih komponenti. Više informacija možete pronaći na sljedećim poveznicama:

- <http://tinyurl.com/TS555N>
- <http://tinyurl.com/BC546A>
- <http://tinyurl.com/BC556A>

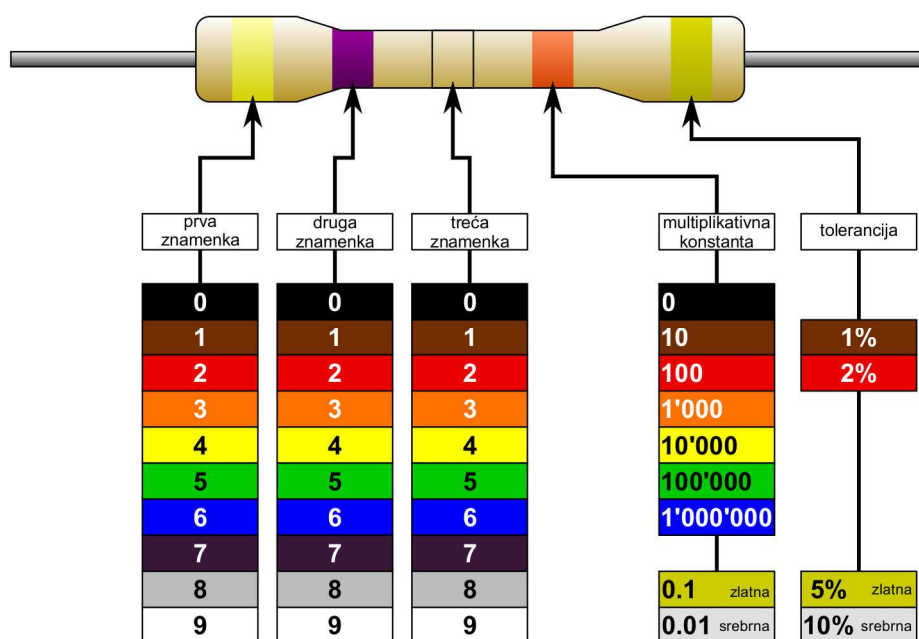

Slika 2: Legenda boja otpornika



TS555

Low power single CMOS timer

Features

- Very low power consumption:
110 μ A typ at $V_{CC} = 5$ V
90 μ A typ at $V_{CC} = 3$ V
- High maximum astable frequency of 2.7 MHz
- Pin-to-pin functionally-compatible with bipolar NE555
- Wide voltage range: +2 V to +16 V
- Supply current spikes reduced during output transitions
- High input impedance: $10^{12} \Omega$
- Output compatible with TTL, CMOS and logic MOS

Description

The TS555 is a single CMOS timer with a very low consumption:

($I_{CC(TYP)}$ TS555 = 110 μ A at $V_{CC} = +5$ V versus
 $I_{CC(TYP)}$ NE555 = 3 mA),

and high frequency:


($f_{f(max.)}$ TS555 = 2.7 MHz versus

$f_{f(max.)}$ NE555 = 0.1 MHz).

Timing remains accurate in both monostable and astable mode.

The TS555 provides reduced supply current spikes during output transitions, which enable the use of lower decoupling capacitors compared to those required by bipolar NE555.

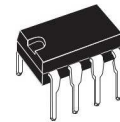With the high input impedance ($10^{12} \Omega$), timing capacitors can also be minimized.



N
DIP8
(Plastic package)




D
SO8
(Plastic micropackage)



P
TSSOP8
(Thin shrink small outline package)

Pin connections (top view)

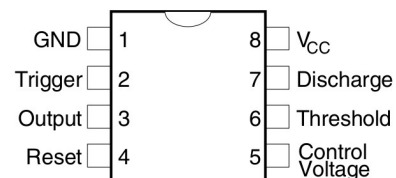


4.2 Astable operation

When the circuit is connected as shown in [Figure 6](#) (pins 2 and 6 connected) it triggers itself and runs as a multi-vibrator. The external capacitor charges through R_A and R_B and discharges through R_B only. Therefore, the duty cycle may be precisely set by the ratio of these two resistors.

In the astable mode of operation, C charges and discharges between $1/3 V_{CC}$ and $2/3 V_{CC}$. As in the triggered mode, the charge and discharge times, and therefore frequency, are independent of the supply voltage.

Figure 6. Application schematic

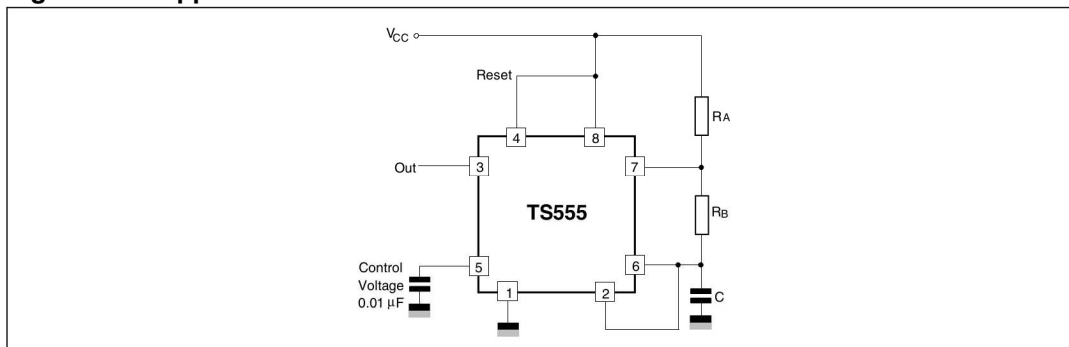

[Figure 7](#) shows actual waveforms generated in this mode of operation.

The charge time (output HIGH) is given by:

$$t1 = 0.693 (R_A + R_B) C$$

The discharge time (output LOW) by:

$$t2 = 0.693 \times R_B \times C$$

Thus the total period T is given by:

$$T = t1 + t2 = 0.693 (R_A + 2R_B) C$$


The frequency of oscillation is then:

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B)C}$$

The duty cycle is given by:

$$D = \frac{R_B}{R_A + 2R_B}$$

Figure 7. Timing diagram

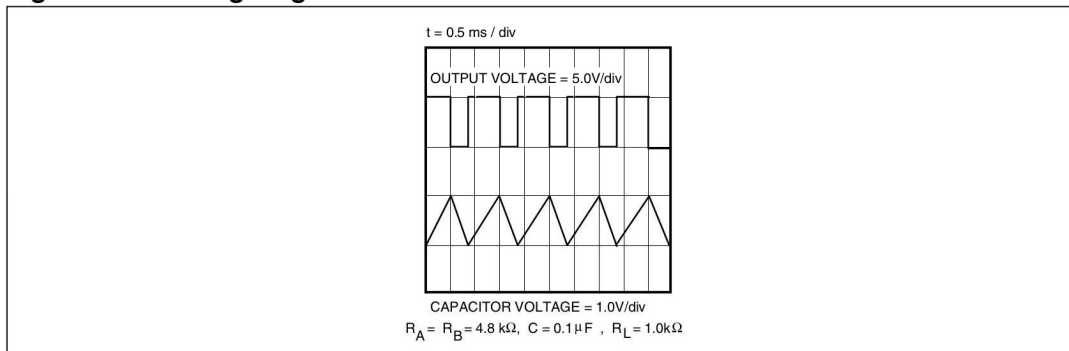




BC556/557/558/559/560

Switching and Amplifier

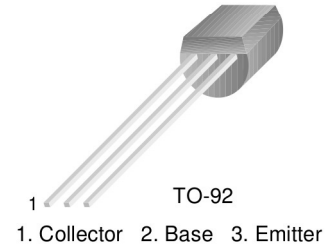- High Voltage: BC556, $V_{CEO} = -65V$
- Low Noise: BC559, BC560
- Complement to BC546 ... BC 550



PNP Epitaxial Silicon Transistor

Absolute Maximum Ratings $T_a = 25^\circ C$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CBO}	Collector-Base Capacitance		
	: BC556	-80	V
	: BC557/560	-50	V
	: BC558/559	-30	V
V_{CEO}	Collector-Emitter Voltage		
	: BC556	-65	V
	: BC557/560	-45	V
	: BC558/559	-30	V
V_{EBO}	Emitter-Base Voltage	-5	V
I_C	Collector Current (DC)	-100	mA
P_C	Collector Dissipation	500	mW
T_J	Junction Temperature	150	$^\circ C$
T_{STG}	Storage Temperature	-65 ~ 150	$^\circ C$

Electrical Characteristics $T_a = 25^\circ C$ unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Typ.	Max.	Units
I_{CBO}	Collector Cut-off Current	$V_{CB} = -30V, I_E = 0$			-15	nA
h_{FE}	DC Current Gain	$V_{CE} = -5V, I_C = 2mA$	110		800	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C = -10mA, I_B = -0.5mA$		-90	-300	mV
		$I_C = -100mA, I_B = -5mA$		-250	-650	mV
$V_{BE(sat)}$	Collector-Base Saturation Voltage	$I_C = -10mA, I_B = -0.5mA$		-700		mV
		$I_C = -100mA, I_B = -5mA$		-900		mV
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE} = -5V, I_C = -2mA$	-600	-660	-750	mV
		$V_{CE} = -5V, I_C = -10mA$			-800	mV
f_T	Current Gain Bandwidth Product	$V_{CE} = -5V, I_C = -10mA, f = 10MHz$		150		MHz
C_{ob}	Output Capacitance	$V_{CB} = -10V, I_E = 0, f = 1MHz$			6	pF
NF	Noise Figure	: BC556/557/558		2	10	dB
		: BC559/560		1	4	dB
		: BC559		1.2	4	dB
		: BC560		1.2	2	dB

h_{FE} Classification

Classification	A	B	C
h_{FE}	110 ~ 220	200 ~ 450	420 ~ 800


BC556/557/558/559/560



BC546/547/548/549/550

Switching and Amplifier

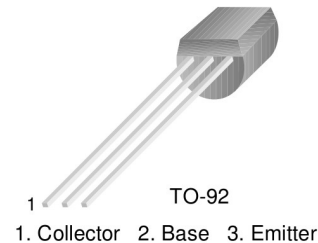- High Voltage: BC546, $V_{CEO}=65V$
- Low Noise: BC549, BC550
- Complement to BC556 ... BC560



NPN Epitaxial Silicon Transistor

Absolute Maximum Ratings $T_a=25^\circ C$ unless otherwise noted

Symbol	Parameter	Value	Units
V_{CBO}	Collector-Base Voltage : BC546	80	V
	: BC547/550	50	V
	: BC548/549	30	V
V_{CEO}	Collector-Emitter Voltage : BC546	65	V
	: BC547/550	45	V
	: BC548/549	30	V
V_{EBO}	Emitter-Base Voltage : BC546/547	6	V
	: BC548/549/550	5	V
I_C	Collector Current (DC)	100	mA
P_C	Collector Dissipation	500	mW
T_J	Junction Temperature	150	$^\circ C$
T_{STG}	Storage Temperature	-65 ~ 150	$^\circ C$

Electrical Characteristics $T_a=25^\circ C$ unless otherwise noted

Symbol	Parameter	Test Condition	Min.	Typ.	Max.	Units
I_{CBO}	Collector Cut-off Current	$V_{CB}=30V, I_E=0$			15	nA
h_{FE}	DC Current Gain	$V_{CE}=5V, I_C=2mA$	110		800	
$V_{CE(sat)}$	Collector-Emitter Saturation Voltage	$I_C=10mA, I_B=0.5mA$ $I_C=100mA, I_B=5mA$		90 200	250 600	mV mV
$V_{BE(sat)}$	Base-Emitter Saturation Voltage	$I_C=10mA, I_B=0.5mA$ $I_C=100mA, I_B=5mA$		700 900		mV mV
$V_{BE(on)}$	Base-Emitter On Voltage	$V_{CE}=5V, I_C=2mA$ $V_{CE}=5V, I_C=10mA$	580	660	700 720	mV mV
f_T	Current Gain Bandwidth Product	$V_{CE}=5V, I_C=10mA, f=100MHz$		300		MHz
C_{ob}	Output Capacitance	$V_{CB}=10V, I_E=0, f=1MHz$		3.5	6	pF
C_{ib}	Input Capacitance	$V_{EB}=0.5V, I_C=0, f=1MHz$		9		pF
NF	Noise Figure : BC546/547/548	$V_{CE}=5V, I_C=200\mu A$		2	10	dB
	: BC549/550	$f=1KHz, R_G=2K\Omega$		1.2	4	dB
	: BC549	$V_{CE}=5V, I_C=200\mu A$		1.4	4	dB
	: BC550	$R_G=2K\Omega, f=30\sim 15000MHz$		1.4	3	dB

h_{FE} Classification

Classification	A	B	C
h_{FE}	110 ~ 220	200 ~ 450	420 ~ 800